

Lab 4: Pipelined Processor

Robert Chen

86266604

3/8/2020

Objective:

The pipelined processor can be broken down into its original 5 components (instruction fetch, instruction decode, execution, memory, writeback) in addition to intermediary registers between each stage that allow for hazard detection and forwarding. Using this pipelined implementation shown in Figure I, instructions can be carried out without any dependencies on the value of other instructions and registers. The result of one component is frequently used as an input to at least one or more other components, with the values stored in a wire, so that new instructions can be loaded in as the previous instruction is still being processed in a further stage.

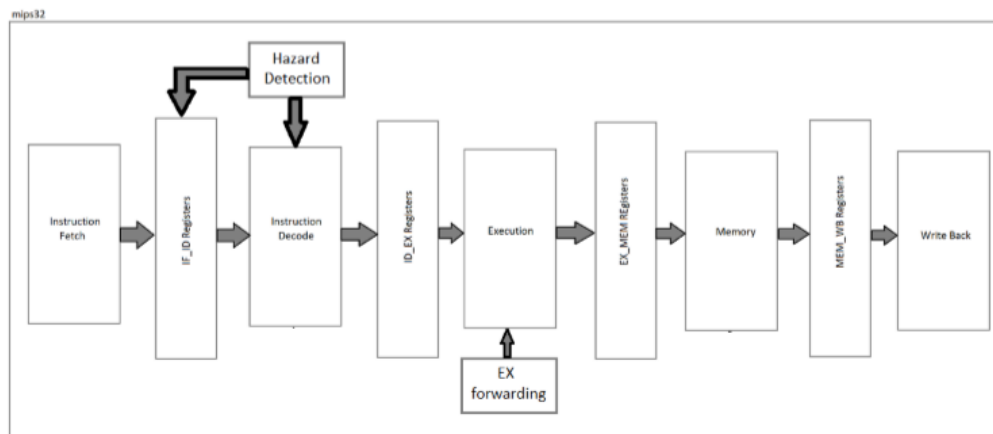


Figure I. Pipelined Processor Structure

Procedure:

IF: For the instruction fetch unit, 2-bit muxes are used to determine the next pc based on whether a branch or jump should be taken or not. Once the next pc is determined, the Data_Hazard input is checked where it returns the next pc if there is no data hazard, or returns the same unchanged pc if there is a data hazard. This is how the pc is “stalled” for one cycle to avoid a data hazard. Otherwise, the pc will just increment for pc+4 as normal and continue to the next instruction.

ID: For the instruction decode unit, the instruction is extracted through the control.v and register file units to know what operation to do and where to store the results. Output data from the memory-writeback unit is used as an input here to the register file. The control unit outputs are also checked against data hazard and control hazard from the forwarding unit to ensure that the values will only be defined if there is no hazard.

EX: For the execution stage, the alu_in2_out output will get the value of the data in id_ex_reg2, the write_back_data, or the ex_mem_alu_result depending on the forwarding condition. The alu_result output will get the processed value of a and b, where a is either the data of id_ex_reg1, write_back_data, or ex_mem_alu_result, and b is the immediate value from the instruction. The selections are based on the alu_src output of control.v and the forwarding conditions.

Forwarding: For the forwarding unit, ForwardA and ForwardB can take values of 10 or 11, with 00 as default. These outputs are used in a 4-bit mux as a selector in the execution stage. Forwarding occurs when there is a potential data hazard.

WB: For the write back mux, the write_back_data (output) will be chosen between the alu result or the memory read data from the memory-writeback unit based on the mem-to-reg output. This result is displayed as the main result, and is also used again as an input to the decode stage.

Reg: For all intermediary registers between each stage, all the input wire data were concatenated into port d and outputted at port q. From there, the concatenated q output was extracted back into its individual wires to be used for the next stage. The individual output wires are named differently so that those data can be processed and the original wires can take on new values of the next instruction.



Simulation Results:

Testbench: (instructions 0-9)




	// load to registers 1 to 10	// instruction	alu result in hex	register content	mem content
○	rom[0] = 32'b10001100000000001000000000000000; // r1 = mem[0]		0	r1 = 00000001	-
○	rom[1] = 32'b10001100000000001000000000000100; // r2 = mem[4]		1	r2 = 0fd76e10	-
○	rom[2] = 32'b10001100000000001000000000000100; // r3 = mem[4]		2	r3 = 0fd76e10	-
○	rom[3] = 32'b100011000000000010000000000001100; // r4 = mem[12]		3	r4 = 14333ffc	-
○	rom[4] = 32'b1000110000000000101000000000010000; // r5 = mem[16]		4	r5 = 321fedcb	-
○	rom[5] = 32'b1000110000000000100000000000010100; // r6 = mem[20]		5	r6 = 80000000	-
○	rom[6] = 32'b1000110000000000110000000000011000; // r7 = mem[24]		6	r7 = 9012fd65	-
○	rom[7] = 32'b1000110000000000100000000000001100; // r8 = mem[28]		7	r8 = abc00237	-
○	rom[8] = 32'b10001100000000001000000000000000; // r9 = mem[32]		8	r9 = b54bc031	-
○	rom[9] = 32'b10001100000000001010000000000100100; // r10 = mem[36]		9	r10 = c187a606	-

Waveform Data:

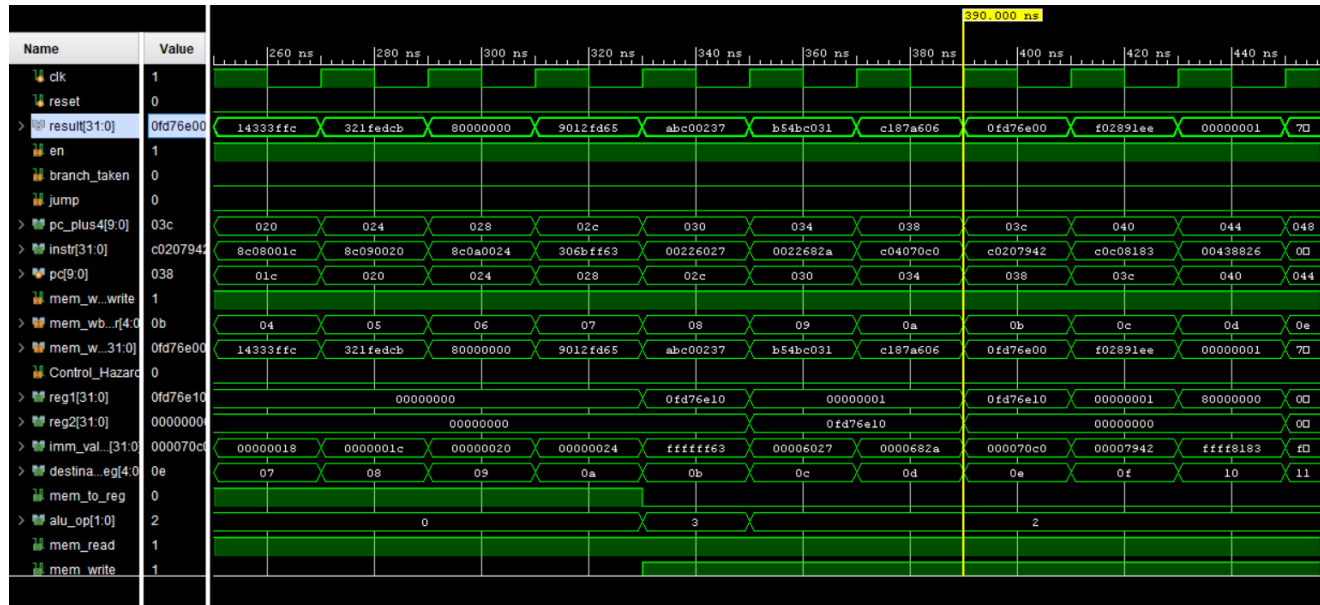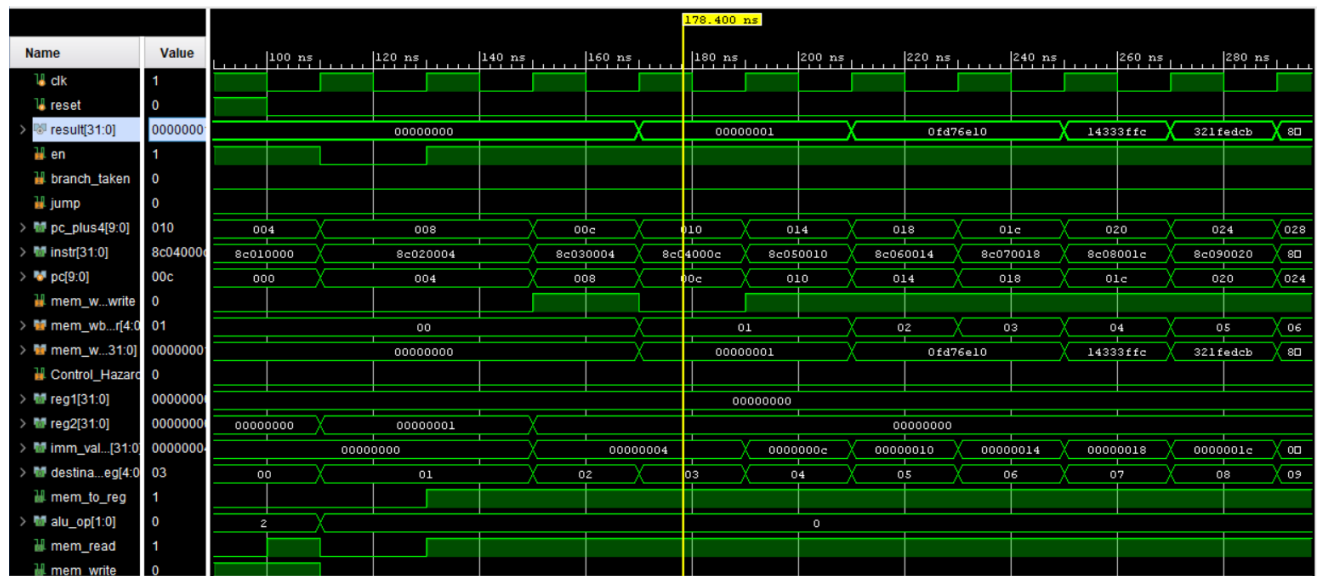In the waveforms below, the written result matches the register content from the instruction memory.



 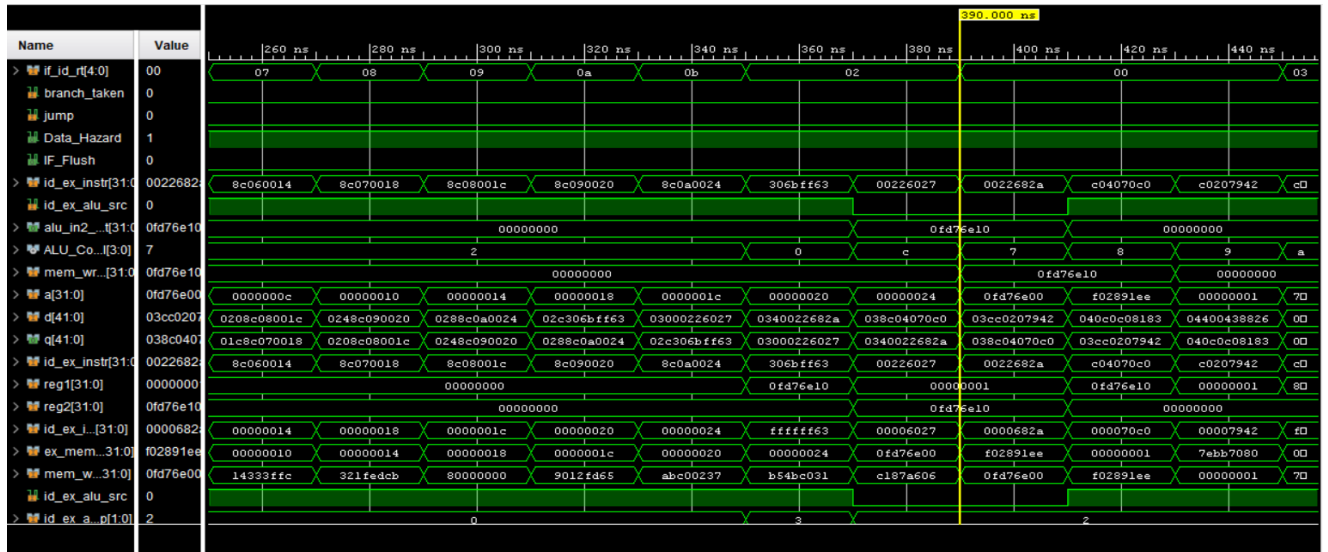 The waveforms below are for instructions 0-9 and show the inputs/outputs of other stages used to determine the resultant data.





Testbench: (instructions 10-27)




```
// no dependency test, no jump
rom[10] = 32'b00110000011010111111111101100011; // andi r11,r3,##f63      0fd76e00      r11= 0fd76e00      -
rom[11] = 32'b0000000001000100110000000100111; // nor r12,r1,r2      f02891ee      r12= f02891ee      -
rom[12] = 32'b0000000001000100110100000101010; // slt r13,r1,r2      1      r13= 1      -
rom[13] = 32'b1100000010000000111000011000000; // sll r14,r2,#3      7ebb7080      r14= 7ebb7080      -
rom[14] = 32'b1100000001000000111100101000010; // srl r15,r1,#5      0      r15= 0      -
rom[15] = 32'b1100000110000001000000110000011; // sra r16,r6,#6      fe000000      r16= fe000000      -
rom[16] = 32'b0000000010000111000100000100110; // xor r17,r2,r3      00000000      r17= 00000000      -
rom[17] = 32'b00000000010001010010000000011000; // mult r17,r1,r2      0fd76e10      r18= 0fd76e10      -
rom[18] = 32'b000000001000011001100000011010; // div r19,r2,r1      0fd76e10      r19= 0fd76e10      -
// store the result in memory
rom[19] = 32'b10101100000010110000000000101100; // sv mem[r0+11] <= r11      2c      -      mem[11]= 0fd76e00
rom[20] = 32'b10101100000011000000000000110000; // sv mem[r0+12] <= r12      30      -      mem[12]= f02891ee
rom[21] = 32'b10101100000011010000000001101000; // sv mem[r0+13] <= r13      34      -      mem[13]= 1
rom[22] = 32'b10101100000011100000000000111000; // sv mem[r0+14] <= r14      38      -      mem[14]= 7ebb7080
rom[23] = 32'b10101100000011110000000000111100; // sv mem[r0+15] <= r15      3c      -      mem[15]= 0
rom[24] = 32'b10101100000010000000000000100000; // sv mem[r0+16] <= r16      40      -      mem[16]= fe000000
rom[25] = 32'b10101100000010001000000000100010; // sv mem[r0+17] <= r17      44      -      mem[17]= 00000000
rom[26] = 32'b10101100000010010000000001001000; // sv mem[r0+18] <= r18      48      -      mem[18]= 0fd76e10
rom[27] = 32'b10101100000010011000000001001100; // sv mem[r0+19] <= r19      4c      -      mem[19]= 0fd76e10
```


Waveform Data:

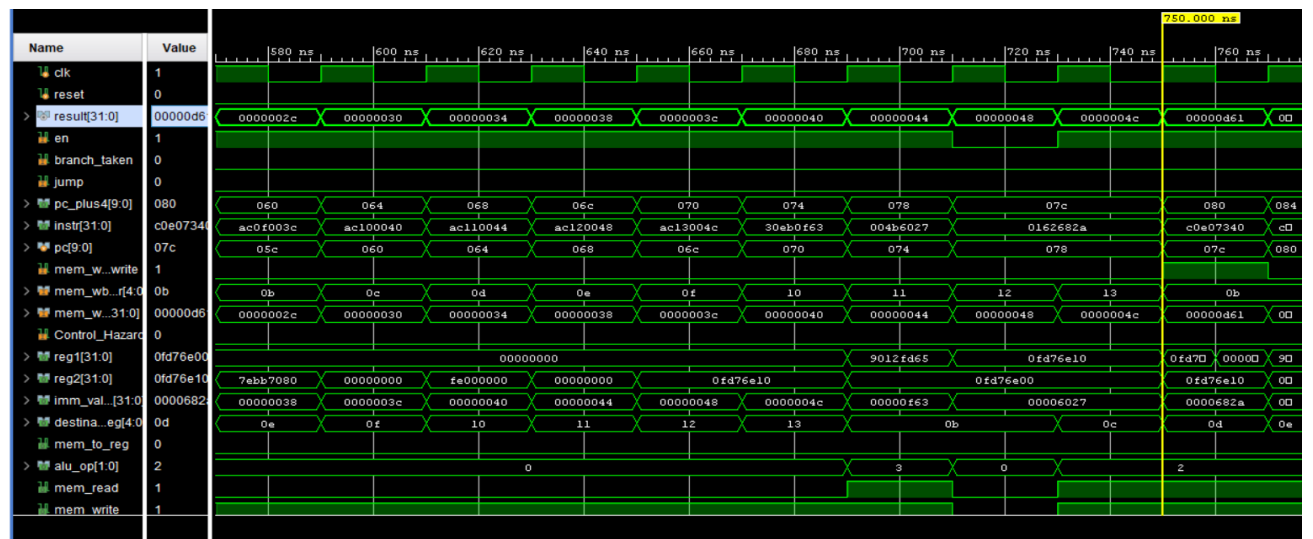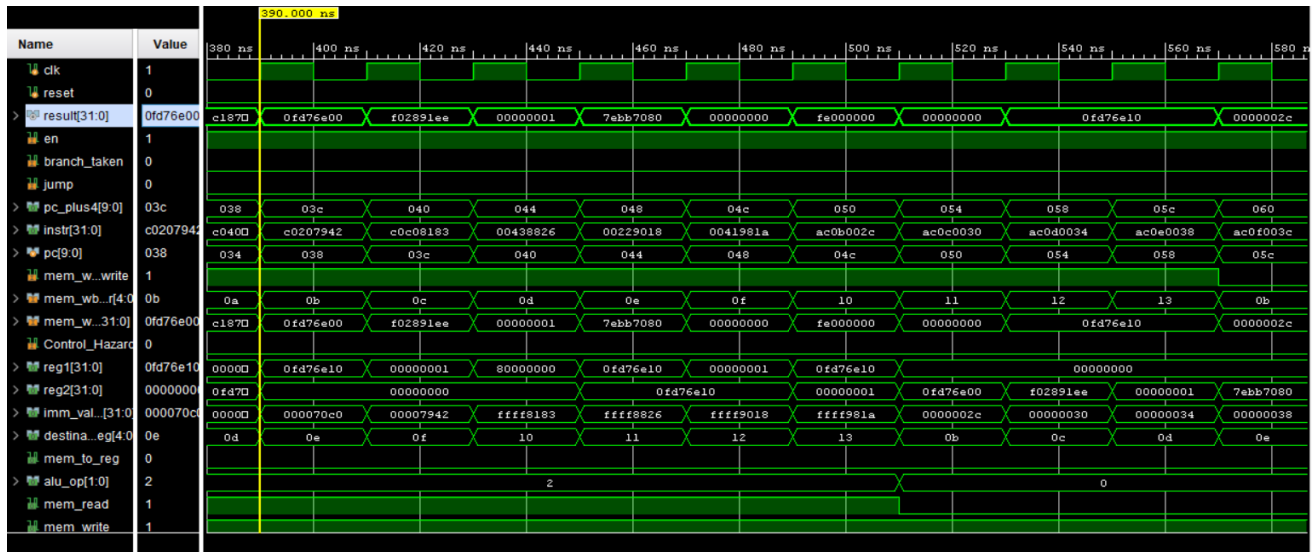In the waveforms below, the written result matches the alu result from the instruction memory.



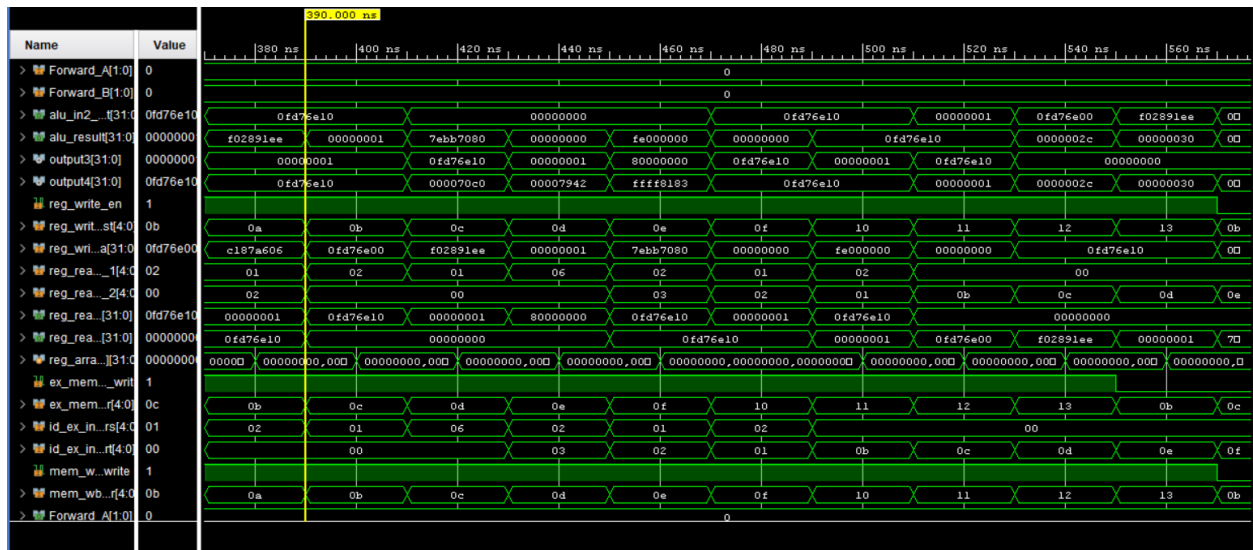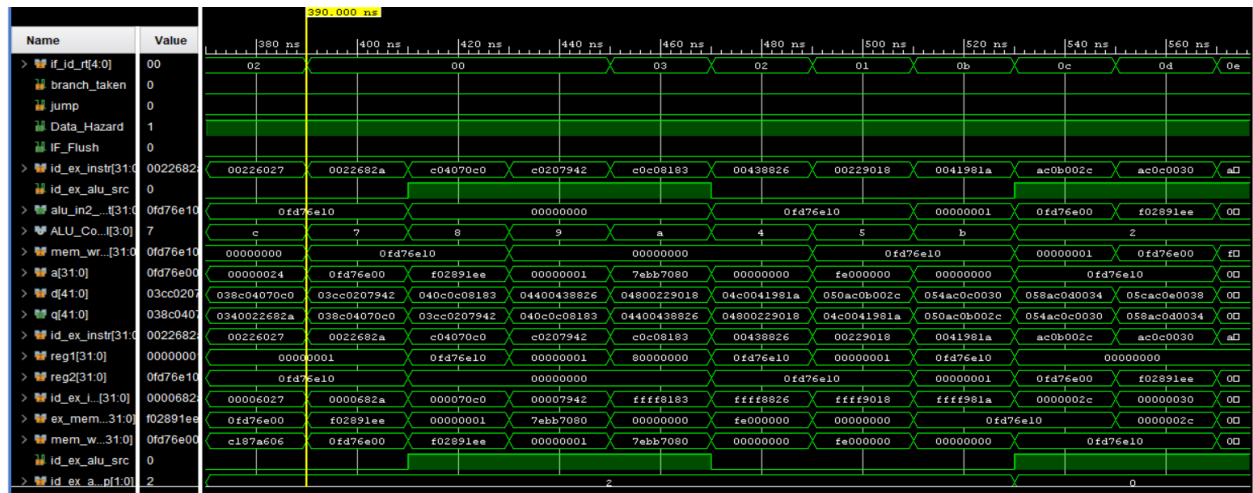 The waveforms below are for instructions 10-18 and show the inputs/outputs of other stages used to determine the resultant data. Similar data for instructions 19-27.




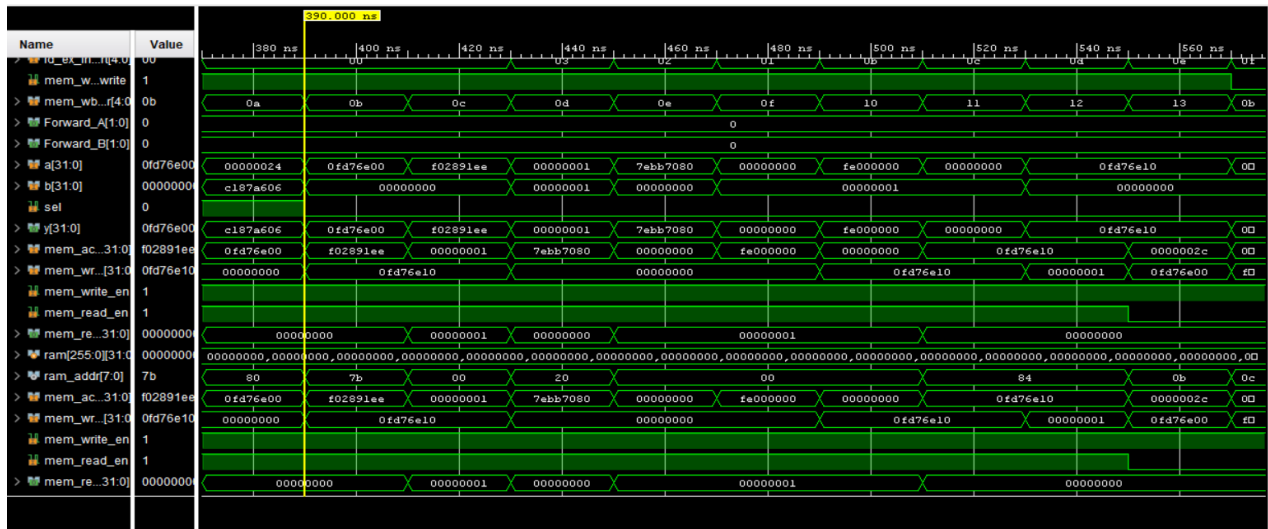

The correct result also displays for instructions beyond 27 and are not shown.

Result Contradiction/Similarity:

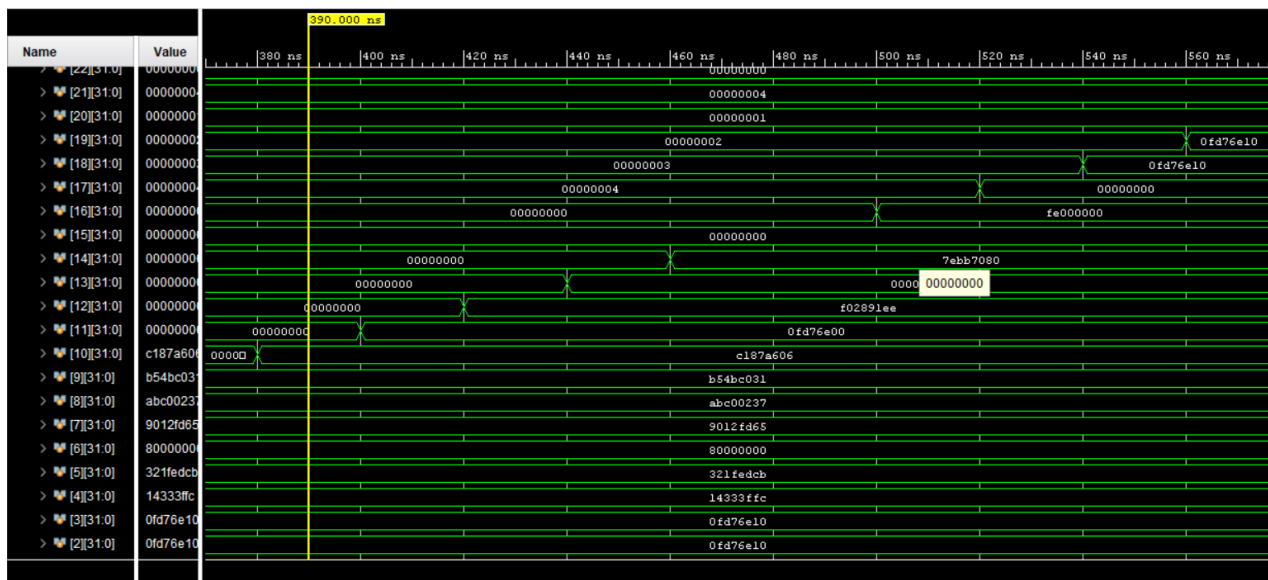The waveform below shows the content of the reg_array.




```

if (uut.data_memory_unit.ram[11]==32'h0fd76e00) $display("NO DEPENDENCY ANDI success!\n"); else $display("NO DEPENDENCY ANDI failed!\n");
if (uut.data_memory_unit.ram[12]==32'hf02891ee) $display("NO DEPENDENCY NOR success!\n"); else $display("NO DEPENDENCY NOR failed!\n");
if (uut.data_memory_unit.ram[13]==32'h00000001) $display("NO DEPENDENCY SLT success!\n"); else $display("NO DEPENDENCY SLT failed!\n");
if (uut.data_memory_unit.ram[14]==32'h7ebb7080) $display("NO DEPENDENCY SLL success!\n"); else $display("NO DEPENDENCY SLL failed!\n");
if (uut.data_memory_unit.ram[15]==32'h00000000) $display("NO DEPENDENCY SRL success!\n"); else $display("NO DEPENDENCY SRL failed!\n");
if (uut.data_memory_unit.ram[16]==32'hfe000000) $display("NO DEPENDENCY SRA success!\n"); else $display("NO DEPENDENCY SRA failed!\n");
if (uut.data_memory_unit.ram[17]==32'h00000000) $display("NO DEPENDENCY XOR success!\n"); else $display("NO DEPENDENCY XOR failed!\n");
if (uut.data_memory_unit.ram[18]==32'h0fd76e10) $display("NO DEPENDENCY MULT success!\n"); else $display("NO DEPENDENCY MULT failed!\n");
if (uut.data_memory_unit.ram[19]==32'h0fd76e10) $display("NO DEPENDENCY DIV success!\n"); else $display("NO DEPENDENCY DIV failed!\n");

```


From the tb_mips32 file, the test cases are checking if ram[11] = 0fd76e00, and so on. The reg_array waveform above shows that I indeed have stored that value 0fd76e00 (also shown in result in previous waveforms) into reg[11], and so on.

 I believe that the tb_mips32 prints out failed cases because the data is being stored into the reg_array instead of the ram, and so the reg_read_data comes out as 0 instead of the expected value. I believe all of the pipelined processor components are working and producing the correct result, but the result is being stored in a different place than the location that tb_mips32 is checking.



From a previous waveform, I found that when reading and writing from memory, the address to write to is 7b and is writing the value 0fd76e10 to ram[7b] instead. It then reads ram[11] as 0 because the value was not stored in ram[11] but in reg_array[11].